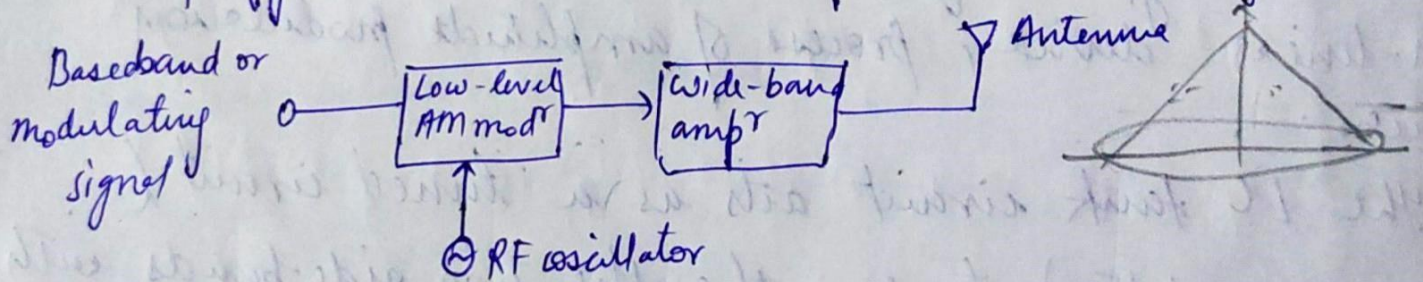


Generation of Amplitude Modulated wave.

Methods of AM generation is broadly classified as.

1) Low-level AM modulation

- Modulation is done at low power
- due to this power amplifiers are needed to boost AM sig to required level.
- AM sig is then applied to a wide-band amp^r to amplify the side-bands of modulated signal.




EX - Square law modulation or Balanced modulator


② High-level Amplitude modulation

- Modulation is done at high power levels
- The baseband sig and the carrier are firstly amplified using wide-band and narrow-band amp^r.


EX - collector modulation method.

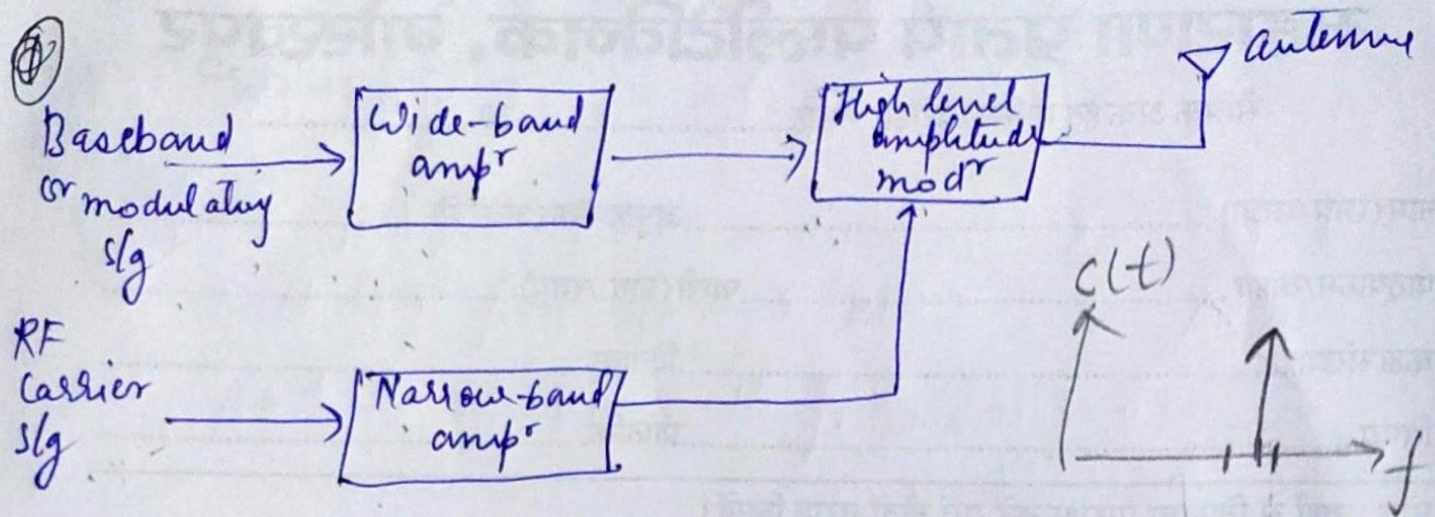

① Square-Law Modulator

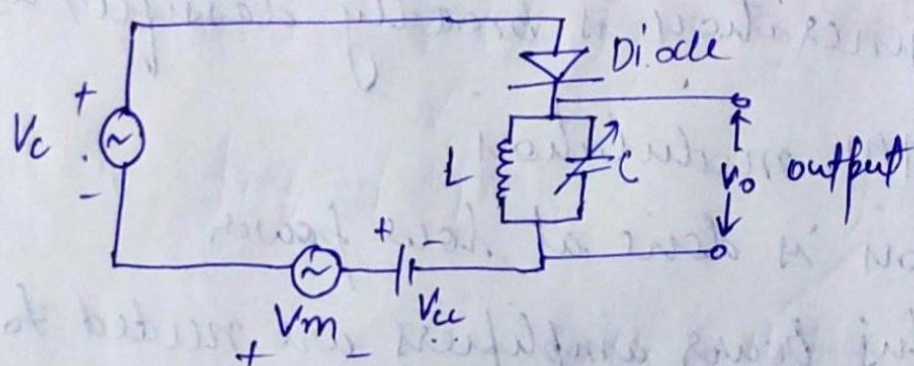

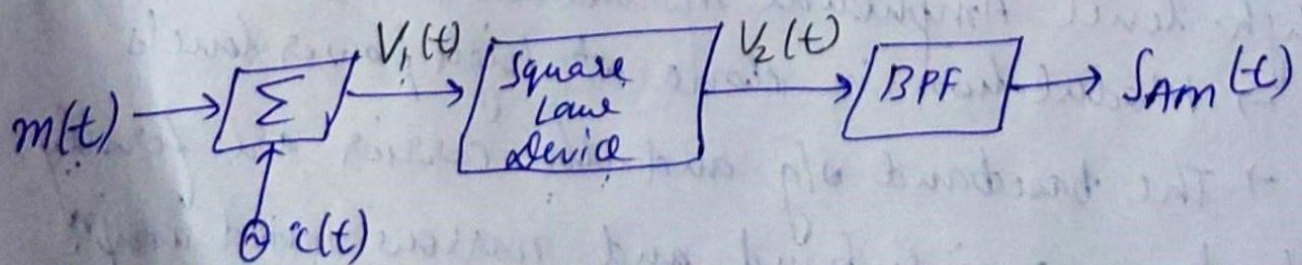- V_{cc} is connected to provide operating voltage to the diode.
- Diode is a non-linear device.
- The working of the circuit is based upon the fact that when two different frequencies are passed through a non-linear device, process of amplitude modulation occurs.
- The LC tank circuit acts as a tuned circuit (band-pass filter) to pass the two sidebands with carrier and reject other frequencies.



A simple block-diagram of Square Law modulator

the $v-i$ relation of a non-linear device

$$i = av + bv^2 + cv^3 + \dots$$

Input to the SLD

$$V_1(t) = m(t) + c(t)$$

$$= m(t) + A_c \cos(2\pi f_c t)$$


output of the SLD

$$V_2(t) = a_1 V_1(t) + a_2 V_1(t)^2 + a_3 V_1(t)^3 + \dots$$


where $a_1, a_2, a_3 \rightarrow$ square law coefficients

$$\Rightarrow V_2(t) = a_1 [m(t) + A_c \cos 2\pi f_c t] + a_2 [m^2(t) + A_c^2 \cos^2 2\pi f_c t + 2 A_c \cdot m(t) \cdot \cos 2\pi f_c t]$$

BW of an AM s/g. is

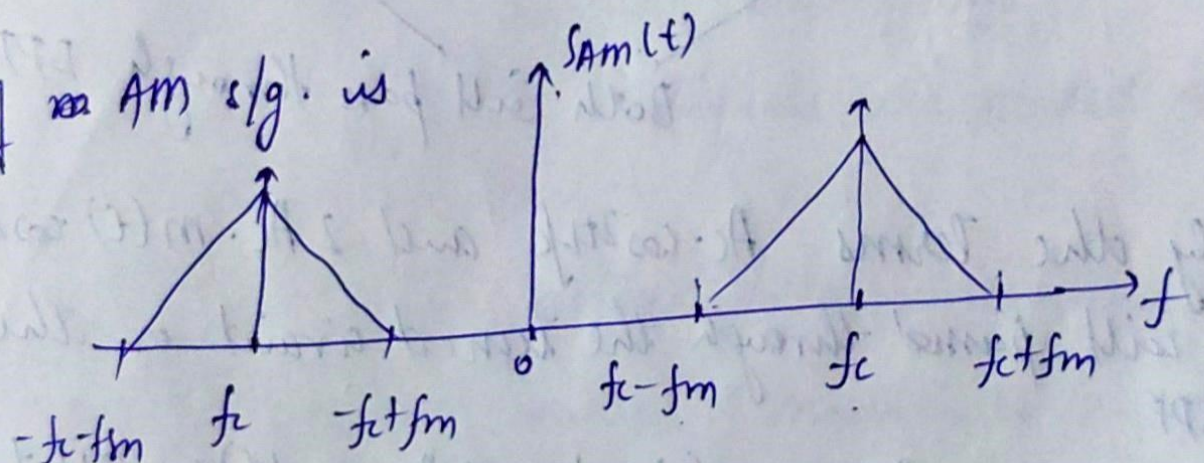

The BPF has the following pass band

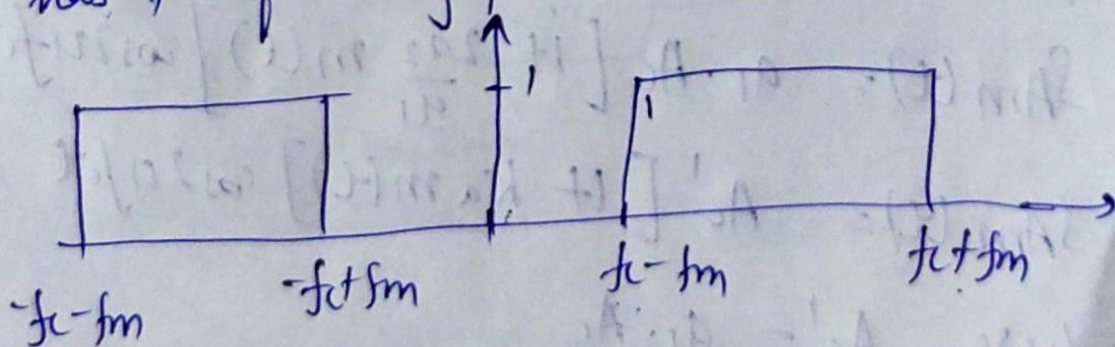

So, $m(t)$ will NOT pass through BPF

$A_c \cos 2\pi f_c t$ will pass through BPF

$m^2(t)$ will NOT pass as $m^2(t) = A_m^2 \cos^2 2\pi f_m t$

$$\cos^2 2\pi f_m t = \frac{1 + \cos 4\pi f_m t}{2} = \frac{1}{2} + \frac{\cos 4\pi f_m t}{2}$$

since $f_c \gg f_m$, $2f_m$ will also NOT pass

$A_c^2 \cos^2 2\pi f_c t$ will NOT pass through BPF

since $\cos^2 2\pi f_c t \rightarrow \frac{1 + \cos 4\pi f_c t}{2} = \frac{1}{2} + \frac{\cos 4\pi f_c t}{2}$

Now $2f_c > f_c + f_m$, hence component $\cos 2\pi(2f_c)t$ will NOT pass through BPF

and $\frac{1}{2}$ is DC with frequency $= 0$.

$m(t) \cdot A_c \cos 2\pi f_c t$ will pass through BPF

as $A_m \cdot A_c \cos 2\pi f_c t \cos 2\pi f_m t$

$$= \frac{1}{2} \cos 2\pi(f_c + f_m)t + \frac{1}{2} \cos 2\pi(f_c - f_m)t$$

freq = $f_c + f_m$

freq = $f_c - f_m$

Both will pass through BPF

So only the terms $A_c \cos 2\pi f_c t$ and $2 A_c m(t) \cos 2\pi f_c t$ will pass through the tuned circuit or the BPF

$$\text{BPF output} = a_1 A_c \cos 2\pi f_c t + a_2 2 A_c m(t) \cos 2\pi f_c t$$

$$S_{AM}(t) = a_1 \cdot A_c \left[1 + \frac{2a_2}{a_1} m(t) \right] \cos 2\pi f_c t$$

$$S_{AM}(t) = A_c' [1 + k_a m(t)] \cos 2\pi f_c t$$

where $A_c' = a_1 \cdot A_c$

and $k_a = \frac{2a_2}{a_1}$