

Topic:- Kirchhoff's laws

[1] Some Important Point :-

- (i) Circuit:- A circuit is a conducting path through which an electric current either flows or is intended to flow.
- (ii) Circuit elements:- The various elements of an electric circuit are called circuit elements. Ex - Inductor, Capacitor, resistor etc.
- (iii) Electric Network:- An electrical network is a combination of various circuit elements connected in any manner.
- (iv) Junction:- Any point in an electric circuit where two or more conductors are joined together is a junction.
- (v) Loop or Mesh:- Any closed conducting path in an electric network is called loop or mesh.
- (vi) Branch:- A branch is any part of the network that lies between two junctions.

[2] Kirchhoff's laws :-
Kirchhoff's extended ohm's law to Complicated Circuits of
gave two laws -

(i) Kirchhoff's first law OR Junction rule \rightarrow

In an electric circuit, the algebraic sum of currents at
any Junction is zero.

OR.

The sum of currents entering a Junction is equal to
the sum of current leaving that Junction.

Mathematically.

$$\sum I = 0$$

- The Current flowing towards the Junction are taken as +ve.
- The Current flowing away from the Junction are taken as -ve

Illustration

By Junction rule


$$\sum I = 0$$

$$\text{or } I_1 + I_2 - I_3 - I_4 = 0$$

$$\text{or } I_1 + I_2 = I_3 + I_4$$

ie Incoming Current = out-going Current

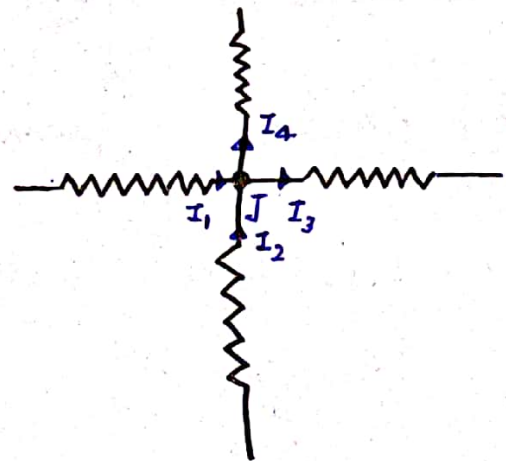First law is also called Kirchhoff's Current law (KCL)



(ii) Kirchhoff's Second law or loop rule:-

Around any closed loop of a network, the algebraic sum of changes in potential must be zero.

OR.

The algebraic sum of the emfs in any loop of a circuit is equal to the sum of the products of currents & resistances in it.

- This law is also known as - Kirchhoff's voltage law (KVL)
Mathematically

$$\sum \Delta V = 0 \quad \text{or} \quad \sum E = \sum IR$$

• Illustration -

for loop ABCFA.

$$\sum IR = I_1 R_1 - I_2 R_2$$


$$\sum E = E_1 - E_2$$

from Kirchhoff's IInd law -

$$E_1 - E_2 = I_1 R_1 - I_2 R_2$$

Similarly for loop CDEFC

$$E_2 = I_2 R_2 + (I_1 + I_2) R_3$$

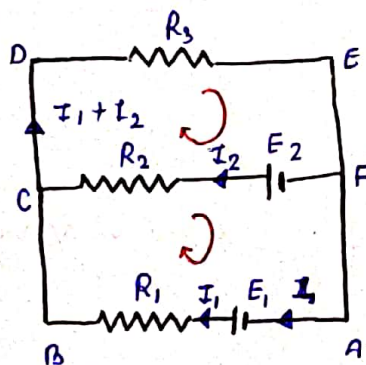

- Take any direction as the direction of traversal (clockwise or anticlockwise).
- The emf of cell is taken as +ve if the dirn of traversal is from its -ve to +ve terminal.
- The emf of cell is taken as -ve if the dirn of traversal is from its +ve to -ve.
- The IR product is taken as +ve if the resistor is traversed in the same dirn of assumed current & vice versa.