
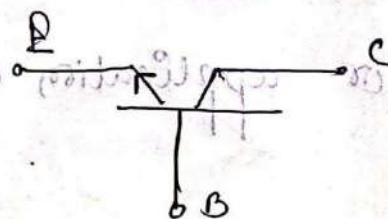
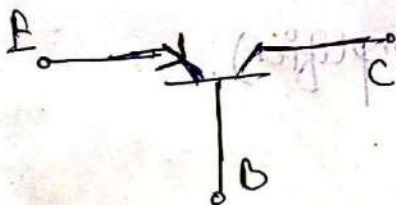
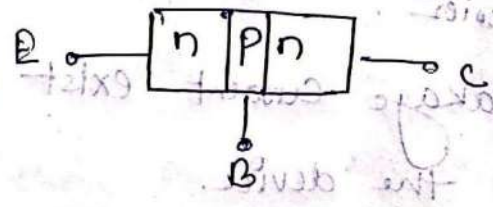


# Bipolar Junction Transistor

- During the period 1904 to 1947, the Vacuum tube was the electronic device.
- And in 1947 transistor was invented by William Shockley, Brattain & Bardeen at Bell Telephone Laboratories.
- It was smaller, lightweight, no heater required.
- Requiring no warm-up period & low operating voltage.

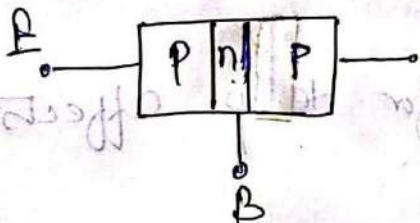
## Construction

- The transistor is a three layer semiconductor device.
- one type of SC (Semiconductor) is sandwiched between other type of SC.
- n-type b/w two (p-type (i.e. pnp)) or p-type is sandwiched b/w two n-type



- Emitter is highly doped to inject maximum no of charge carriers to base.
- Base is lightly doped to reduce the recombination & thus  $I_c$  (Collector Current).
- So, Doping of  $E > C > B$
- Collector is provided with largest area to reduce heat dissipation.
- Base with smallest area to reduce transit time (time taken by charge carrier to move from E to C).
- So for Area,  $C > E > B$ .
- Low  $\rho$  resistance.
- High  $\rho$  resistance.
- Bipolar device (Because majority & minority both are responsible for conduction).
- Noisy device due to presence of minority charge carrier.
- Leakage current exist & therefore temp. affects the device.
- Major application as amp<sup>r</sup> (amplifier).




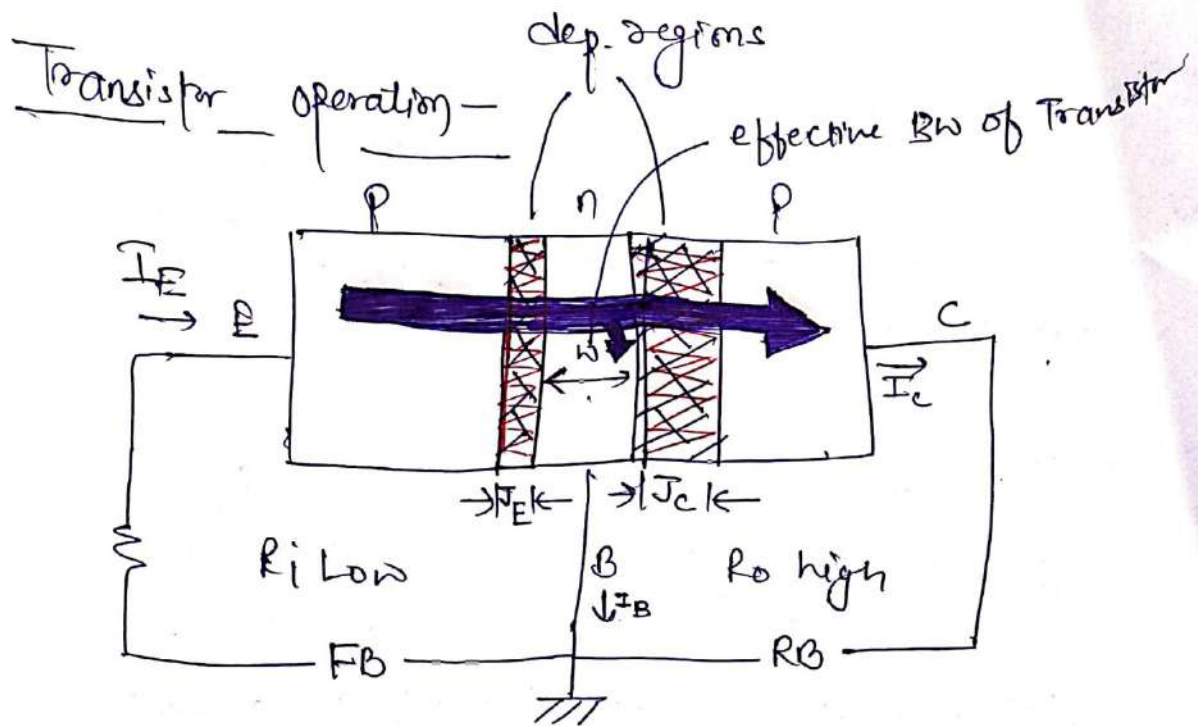

- The widths of dep layer, indicating clearly which junction is FB & which is RB.
- A large no of maj charge carriers will diffuse across the FB P-n junction into n-type material.
- Since the sandwiched n layer is very thin & has low conductivity (less doping), a very small no of charge carrier will recombine with base (at base) results  $I_B$ .
- And now after crossing  $J_E$ , majority charge carrier of p layer (i.e holes) became minority at n layer (holes are minority for n layer sc).
- And now for minority there is no restriction for minority even in R.B.  
so they will cross  $J_C$  & reaches at collector



## Working of pnp transistor -

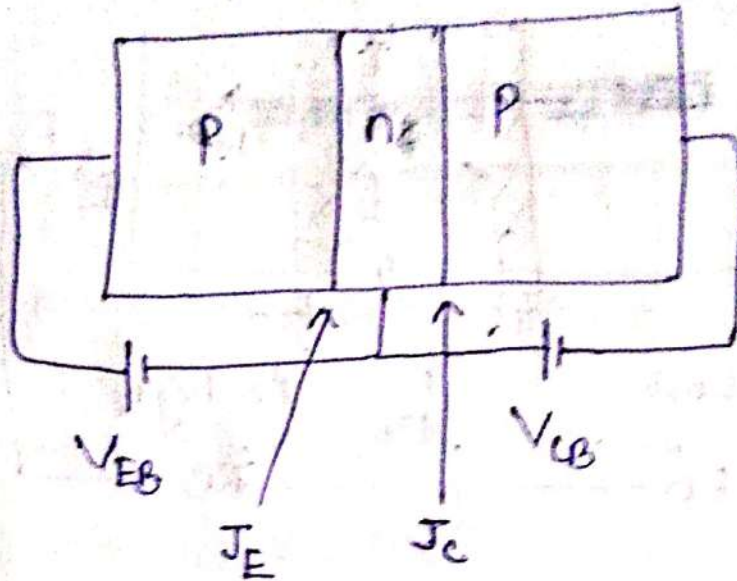

→ As holes are majority charge carrier in P (Emitter layer) &  $p \rightarrow n$  (i.e.  $J_E$ ) is in FB ~~so~~ & holes in Emitter will be repel by  $V_{EB}$ . So they will flow towards  $J_E$ . This constitutes the Emitter current  $I_E$ .

→ As holes combine with  $e^-$  of base. base is lightly doped so only few holes (less than 5%) ~~so~~ combine with  $e^-$ . This constitutes the Base current  $I_B$ .

→ Remaining holes cross the  $J_C$  which is in FB. But holes are minority in Base so they (holes) cross  $J_C$  & reaches Collector constitutes  $I_C$ .

→ So, basically we are controlling current b/w E & C by applying proper  $I_B$ .



## Biasing of a Transistor

By applying a proper DC voltage across different terminals of transistor, Biasing can be done.

The four possible ways of Biasing

Cases	$J_E$	$J_C$	Region of operation
i)	FB	RB	Active
ii)	FB	FB	Saturation
iii)	RB	RB	cut off
iv)	R.B	FB	Inverted

## Transistor Configuration -

These are three terminals, (i.e. E, B, C).

So we can give i/p in any two terminal & take o/p with other two terminal (with a common terminal b/w i/p & o/p).

So depending upon common terminal b/w i/p & o/p. There are three terminals ways


- i) Common Base Configuration
- ii) Common Collector "
- iii) " Emitter "


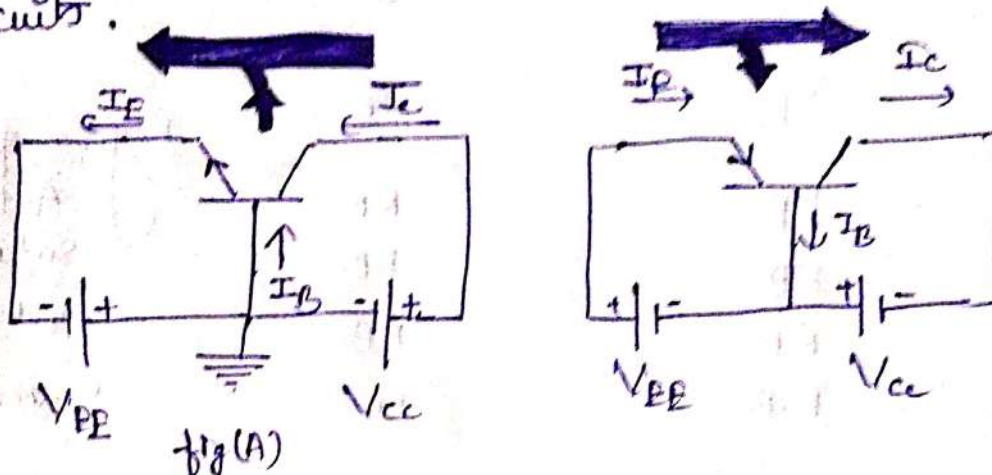
## i) Common Base Configuration

Here  $i_p$  is applied b/w (between) Emitter (E) & Base (B). & o/p is taken b/w B & Collector (C).

Base is common to both  $i_p$  &  $o/p$  circuit.



a CB (Common Base) npn transistor (tr) shown in figure (A) & cb, pnp tr in fig (B).

### Current amplification factor

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \bigg|_{V_{CC} = \text{constant}}$$

where  $\Delta I_C =$   
change in  $I_C$   
 $\Delta I_E =$  change in  $I_E$

$\alpha$  is the ratio of o/p current to the  $i_p$  current.

In case of CB,  $I_E$  is  $i_p$  current &  $I_C$  is o/p current.

$\alpha$  ranges from 0.90 to 0.99



## Expression for Collector Current -

→ As we all know whole  $I_E$  doesn't go to the collector.

→ Because some of its <sup>charge carrier</sup> recombine at base region due to  $e^-$ -hole recombination gives rise to base current.

→ Since the  $I_C$  is  $R_C$  so a leakage current <sup>minority</sup> will also flow from  $C$  to  $B$  (due to  $I_{CBO}$  majority)

So, from above discussion it is clear,

$$I_E = I_B + I_C \quad \text{--- (1)}$$

Some of Emitter charge carrier recombine with base

The charge carrier of  $E$  which remain after recombination.

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (2)}$$

Leakage current due to minority charge carriers.


from eq<sup>n</sup> (1) & (2)

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C(1 - \alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \left( \frac{\alpha}{1 - \alpha} \right) I_B + \left( \frac{1}{1 - \alpha} \right) I_{CBO}$$

## Characteristics of $C_{B1}$ :-

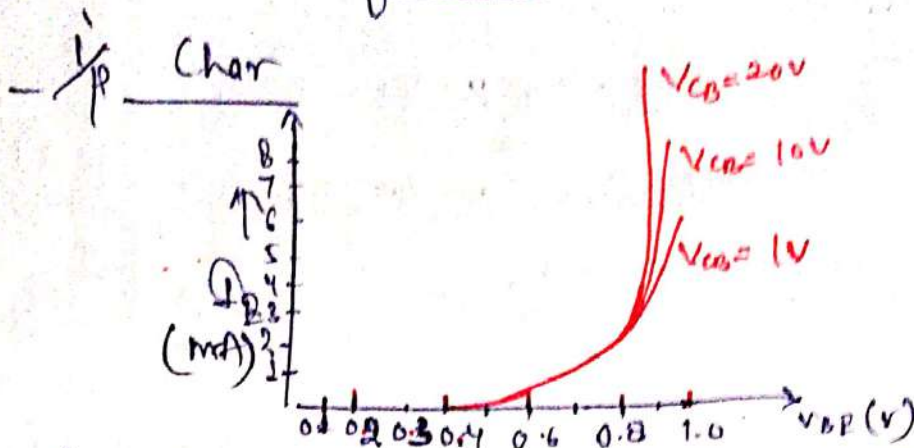

→ It actually relates  $I_P$  current  $I_E$  to  $I_P$  voltage  $V_{BE}$  for various level of  $V_{CB}$ .


→ from above graphs we can conclude that -

→  $I_E \uparrow$  (increases) rapidly with small  $\uparrow$  in  $V_{EB}$  which means  $R_i$  ( $I_P$  resistance is low).

→  $I_E$  is almost independent to  $V_{CB}$ .
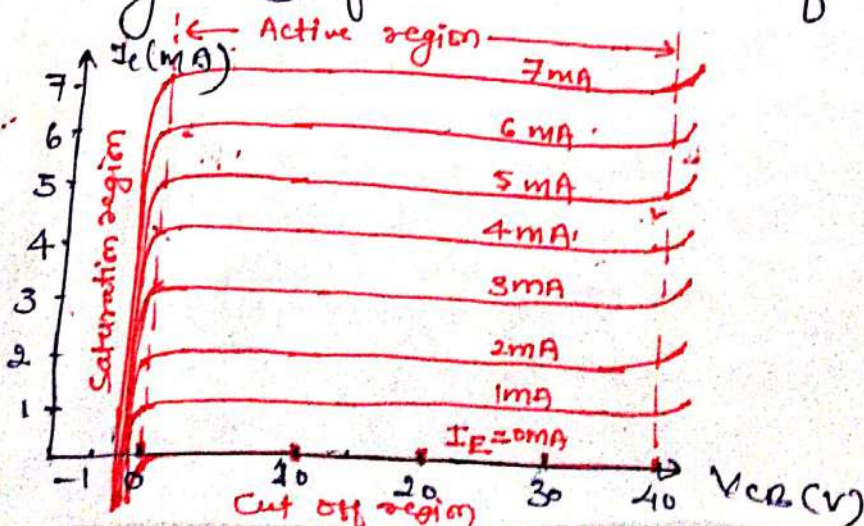
## $O_P$ Char


It actually relates  $O_P$  current  $I_C$  to the  $O_P$  voltage  $V_{CB}$  for various level of  $I_B$ .









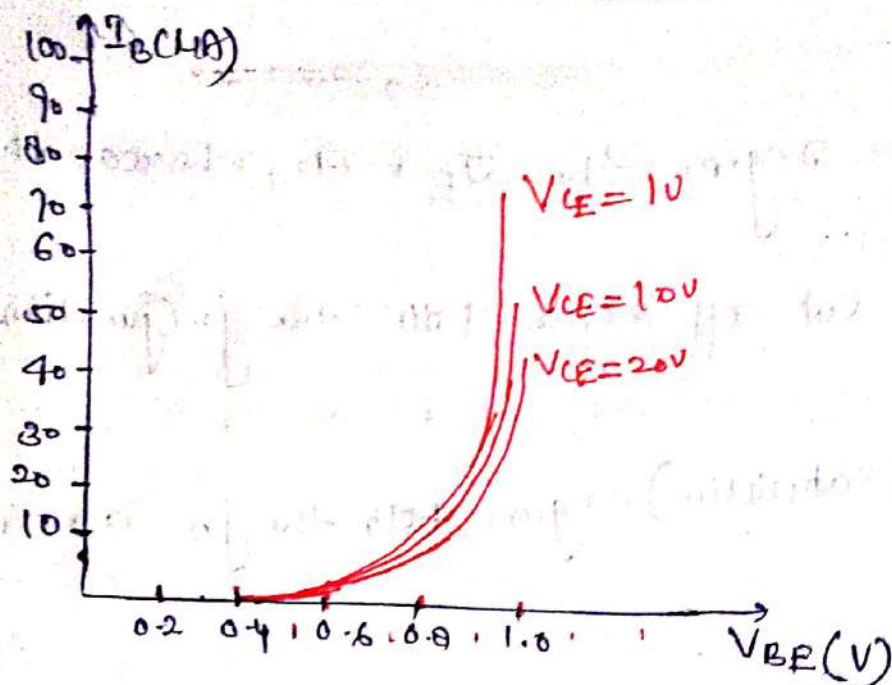


ip char

amplification factor for CE

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

similar as  $\alpha$  for CB  
both are ratio of o/p  
current to the i/p  
current.

CC Configuration

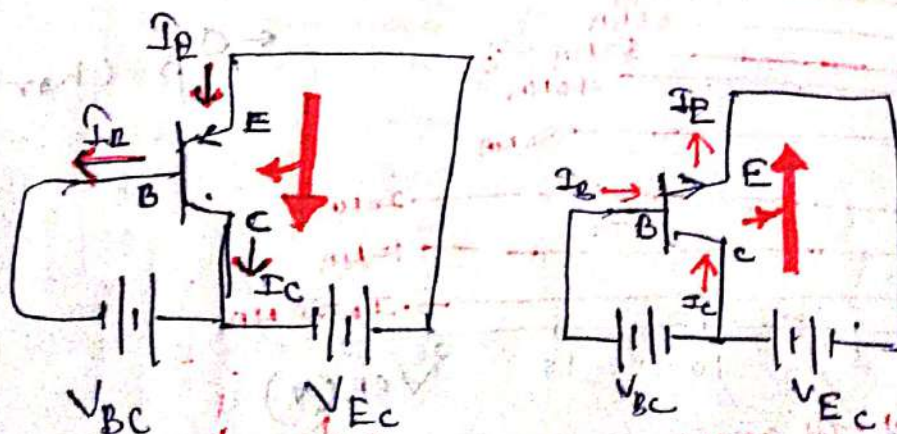



- The third & final configuration is CC.
- Collector is connected in same manner as Emitter, so from design point of view there is no need of set of CC char.
- It can be designed using CE configuration.
- for all the practical purpose, the o/p char of the CC configuration are same as CE.
- the o/p char will be plot of  $I_E$  vs  $V_{CE}$  for range of  $I_B$ .
- the i/p char will be plot of  $I_B$  vs  $V_{BE}$ .

~~The~~  
Amplification factor -

$$V = \frac{\Delta I_E}{\Delta I_B}$$

———— Chapter Over ————

H.W

- try to find out the relation b/w amplification factor of CB, CE & CC (i.e. relation b/w  $\alpha$ ,  $\beta$  &  $r$ ).



Goklani

R. Goklani