
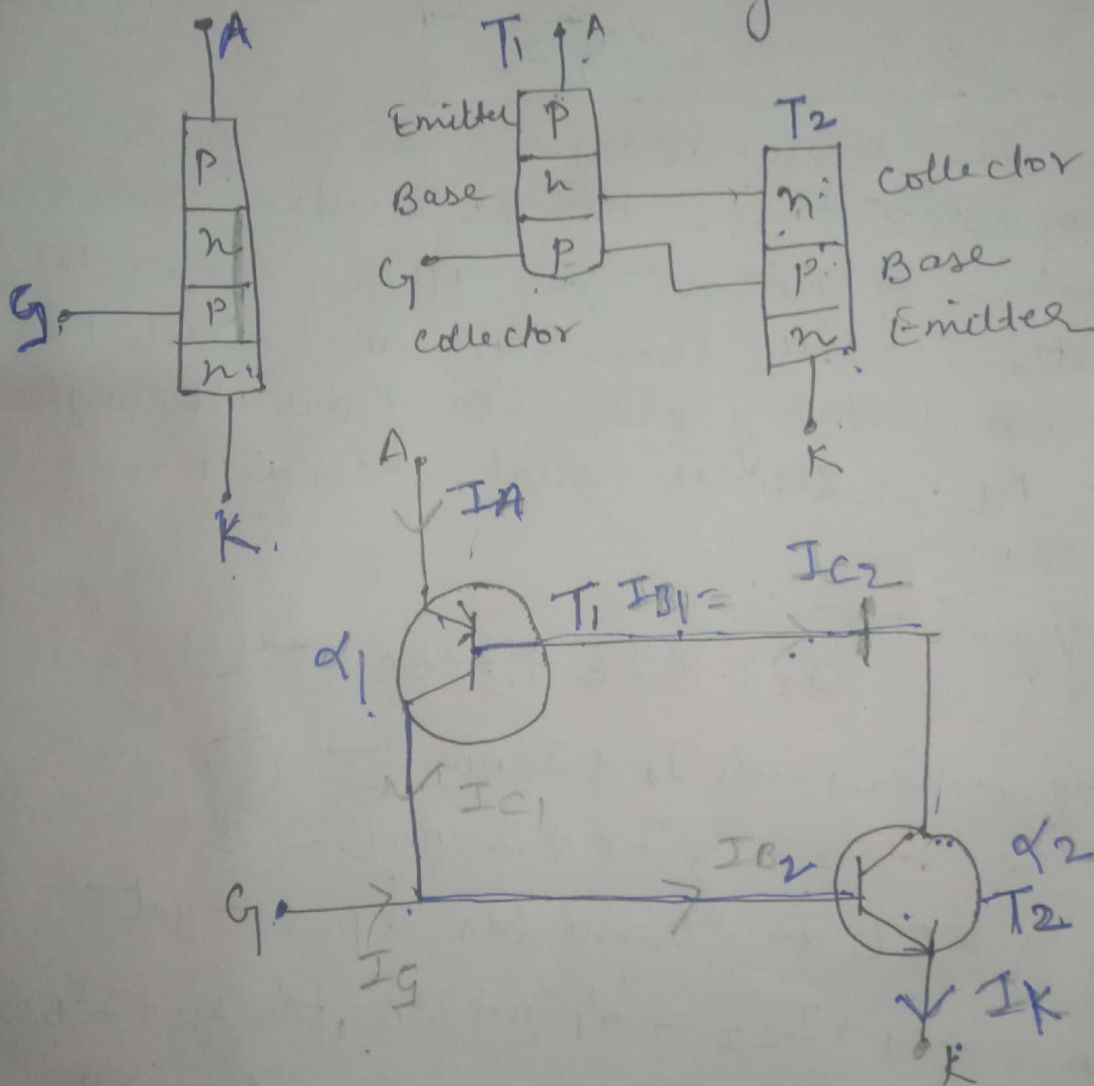


Two Transistor Analogy of Thyristor:-

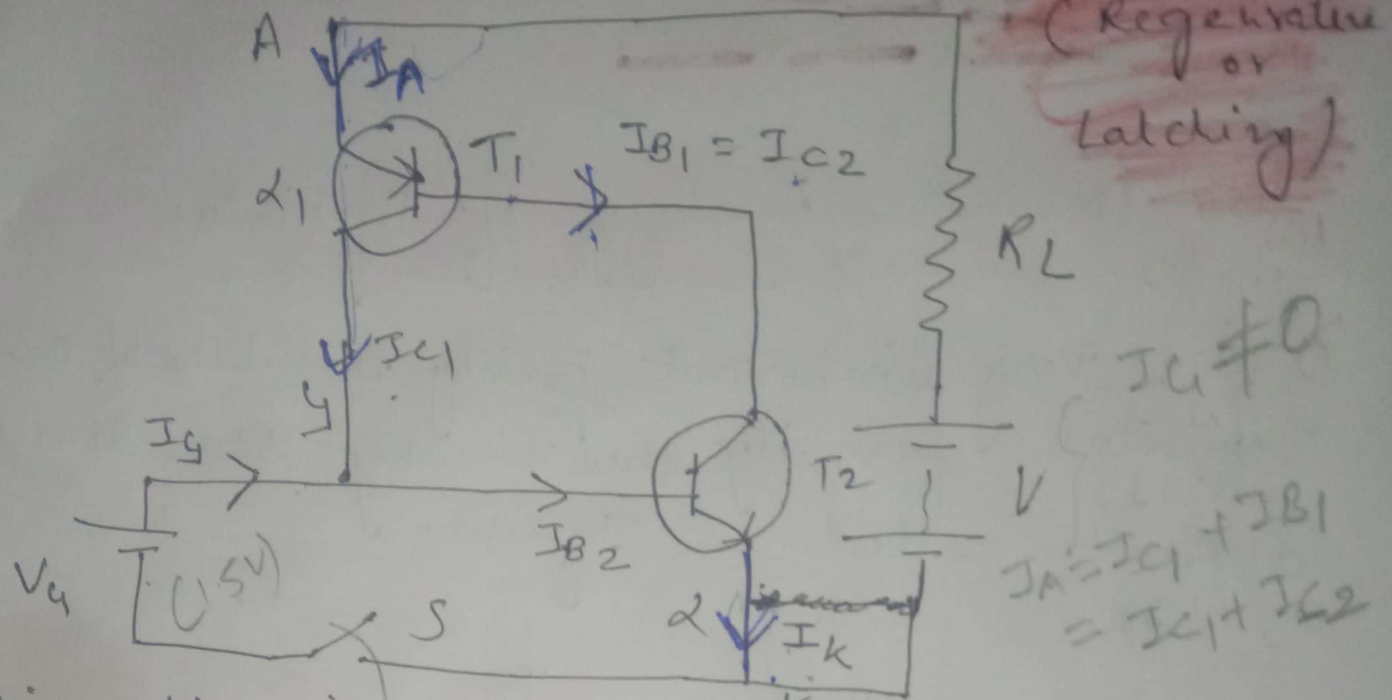SCR is very important family member of a Thyristor family that is why sometimes SCR is called as Thyristor.



NOTE:- It is clear that collector of each transistor is coupled to the base of the other, thereby making a positive feedback loop.



This action is accumulative since an increase of current in one transistor causes an increase of current in other transistor. As a result, both transistor are drive to saturation, and heavy current flows through the load R_L . Under such conditions SCR closes.

For any transistor

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (1)}$$

From CK diag:— $I_{C1} = \alpha_1 I_A + I_{CBO1} \quad \text{--- (2)}$

$$I_{C2} = \alpha_2 I_K + I_{CBO2} \quad \text{--- (3)}$$

Now applying KCL in transistor Q_1 we get—

$$I_A = I_{C1} + I_{C2} = \alpha_1 I_A + I_{CBO1} + \alpha_2 I_K + I_{CBO2} \quad \text{--- (4)}$$

Now, $I_K = I_A + I_G \quad \text{--- (5)}$ put eq (5) into eq (4)

$$I_A = \frac{\alpha_2 I_G + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$

Anode current

SCR TURN ON METHOD



① - By rising temperature [Thermal Triggering]

$$I_A = \frac{\alpha I_G + I_{CBO1} + I_{CBO2}}{[1 - (\alpha_1 + \alpha_2)]}$$

As we ↑ temperature $(\alpha_1 + \alpha_2) \rightarrow 1$, I_A current will increase and SCR will trigger.

② By light triggering Method :- [Optical triggering]

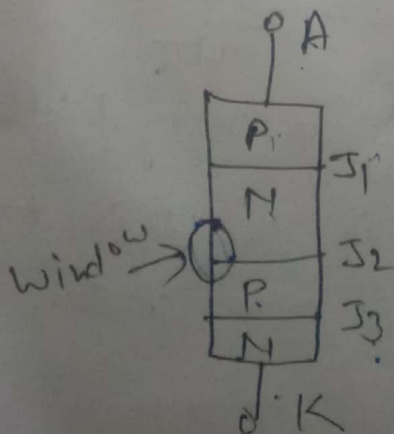
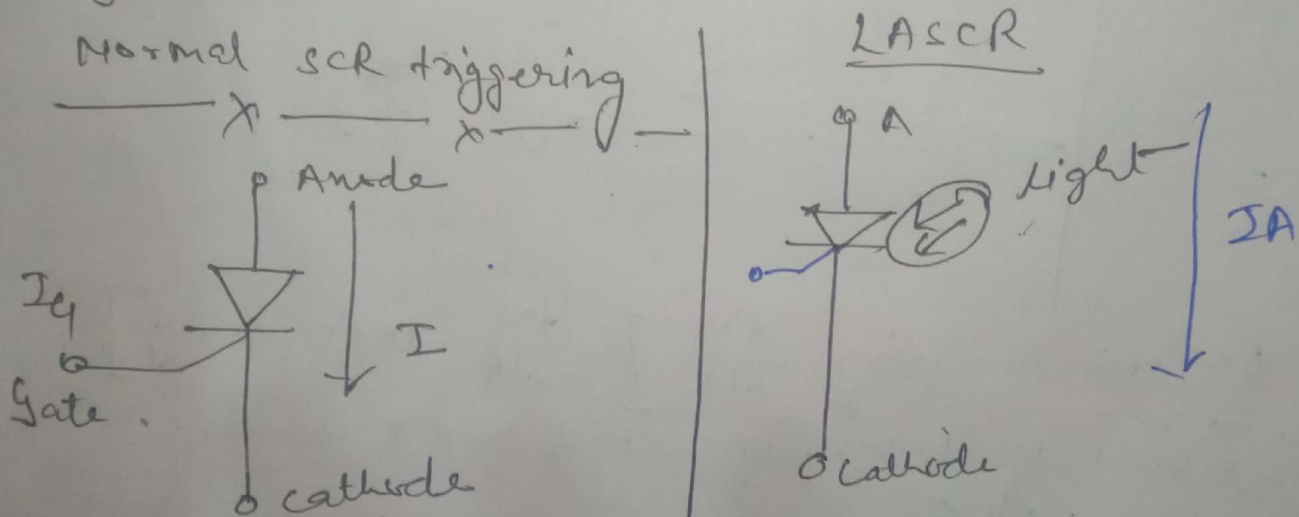
We discuss here about [LASCR]
Light Activated SCR.



due to light coming from window at J_2 the EHPs are generated and J_2 junction diminishes, current starts flowing from Anode to Cathode


③ By high voltage : \overline{F}

[forward voltage triggering]

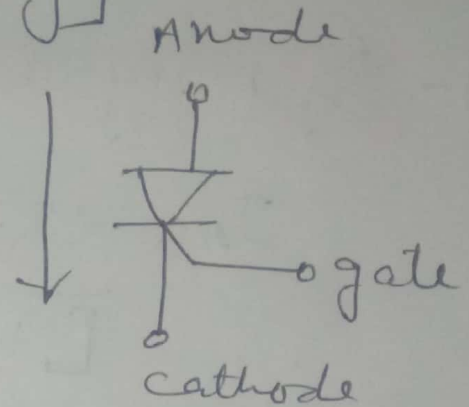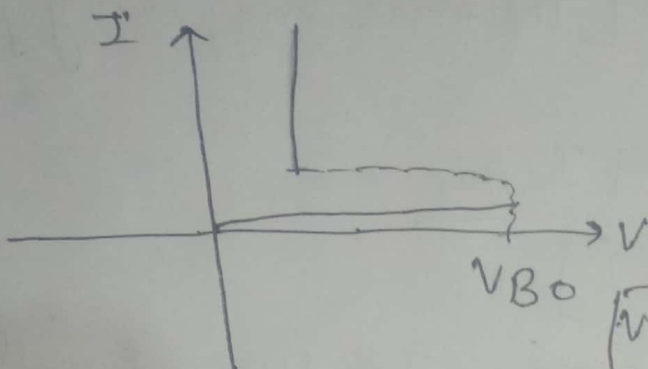


Where V_{BO} - Forward Break over voltage.

④ By Gate Current :- [gate triggering]

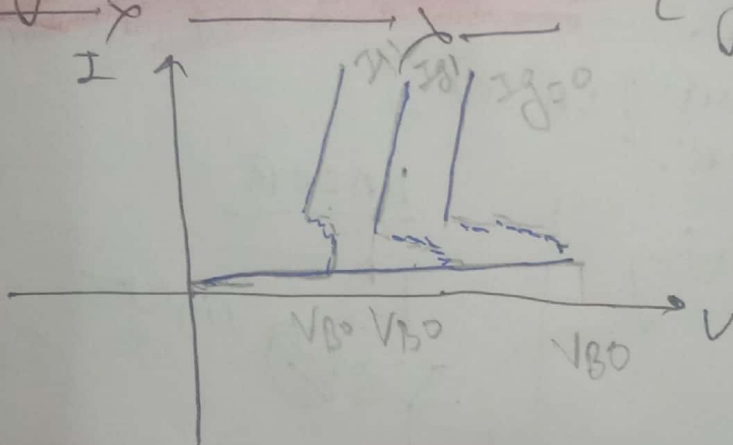

⑤ By increasing $\frac{dV}{dt}$ [$\frac{dV}{dt}$ triggering]


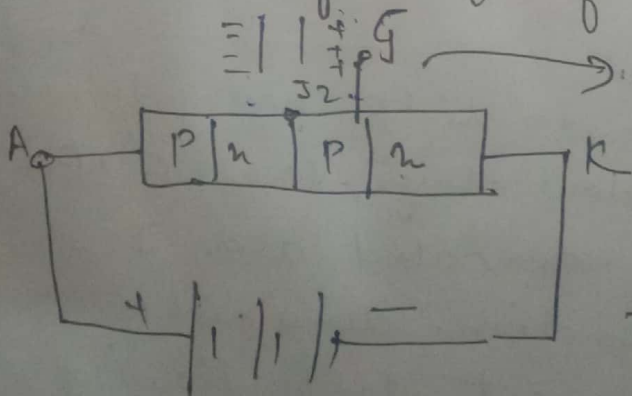
$\frac{dV}{dt} \rightarrow$ rate of change of voltage w.r.t time.



$$I_c = C \frac{dV}{dt}$$

If $\frac{dV}{dt}$ is very high the I_c is sufficient to turn ON SCR.

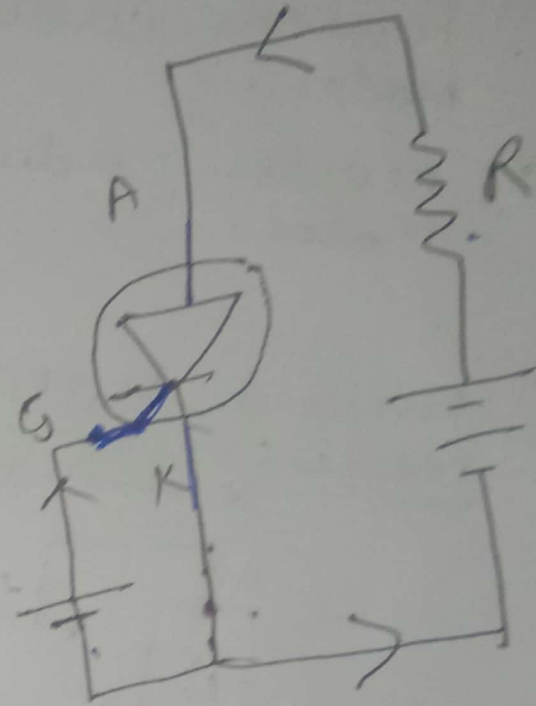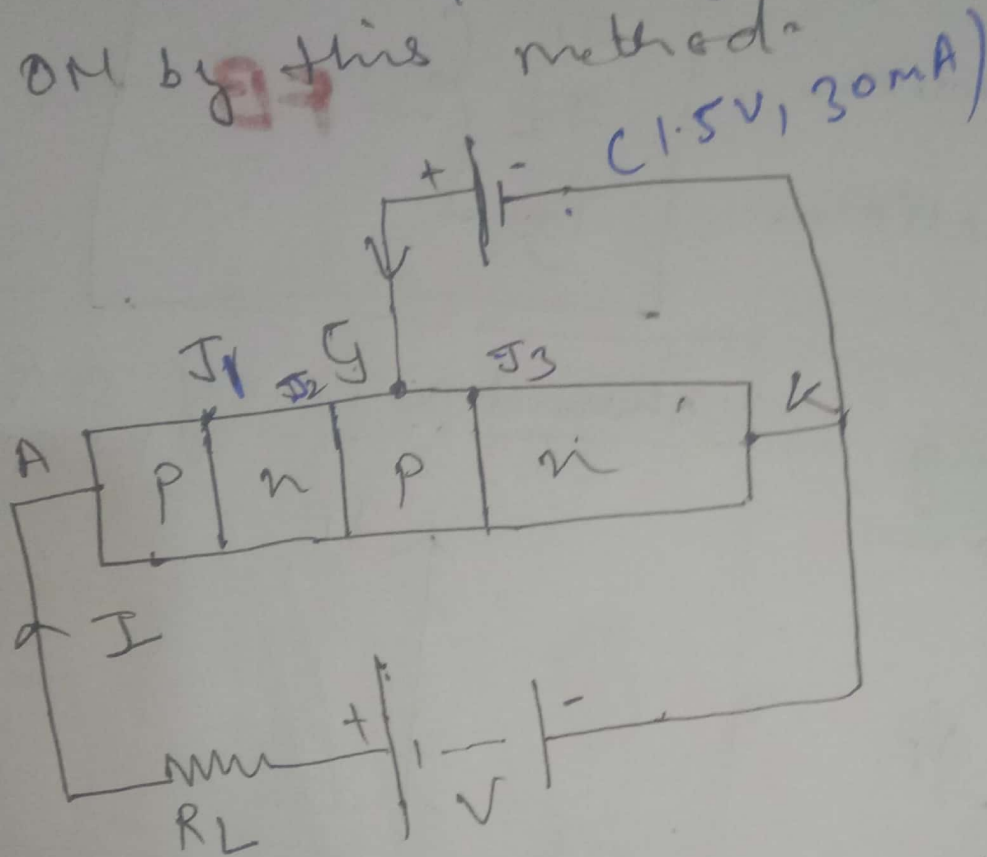increase. Generally SCR is turned ON by this method.



NOTE :- By applying +ve voltage at Gate terminal SCR starts conducting heavily. (Typically 1.5V, 30mA)

(2) To operate SCR Junction J_1 , J_2 and J_3 should be in Fwd bias.

J_1 } F.B.
 J_2 }
 J_3 }