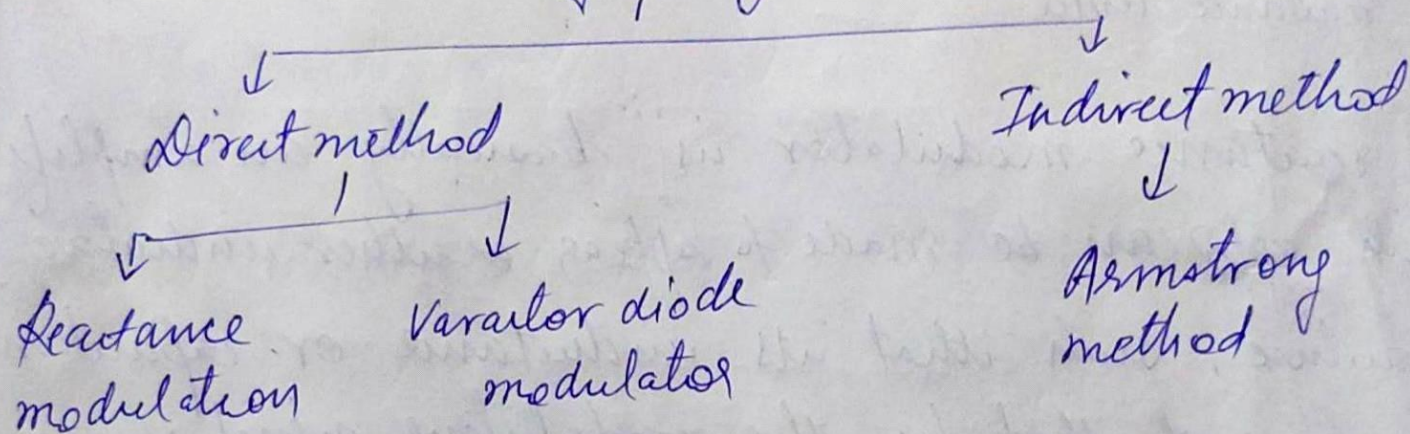


Frequency Modulated wave generation

Methods of FM generation



①. Parameter Variation Method (Direct method)

→ In this method the modulating (msg) signal is directly used in the modulation of the carrier.


→ The carrier signal is generated by an electronic oscillator. The oscillator uses parallel L-C circuit and the frequency of oscillation of the carrier is given as

$$\omega = \frac{1}{\sqrt{LC}}$$

The carrier frequency ω_c can be made to vary according to the message signal $m(t)$, if L or C ^{is} ~~are~~ changed depending upon $m(t)$. Such an

Oscillator whose frequency is controlled by a modulating voltage is called voltage controlled oscillator (VCO).


a) Reactance Modulator

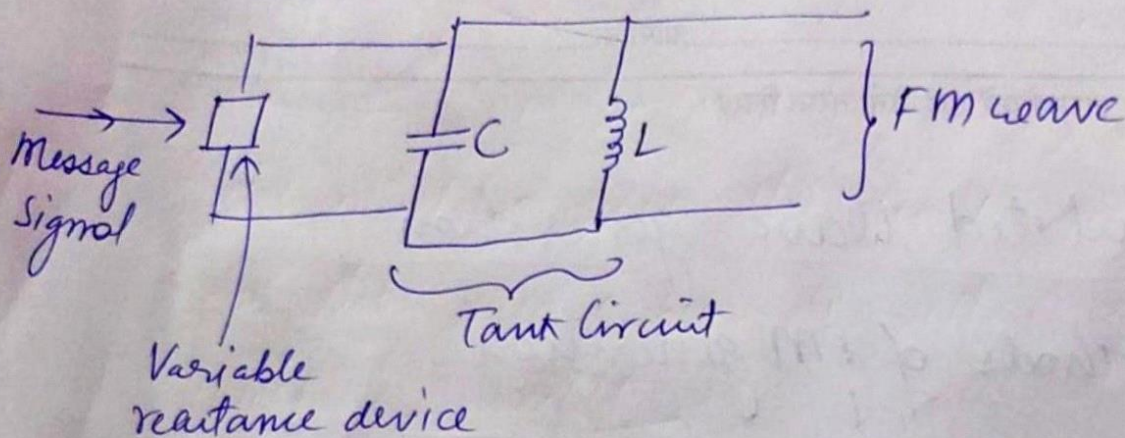

→ A reactance modulator is basically an amplifier which ~~can~~ can be made to ~~appear~~ appear either inductive or capacitive, such that its inductance or capacitance can be controlled by the modulating signal.

→ In the reactance modulator, a transistor or FET is operated as a variable reactance (inductive or capacitive).

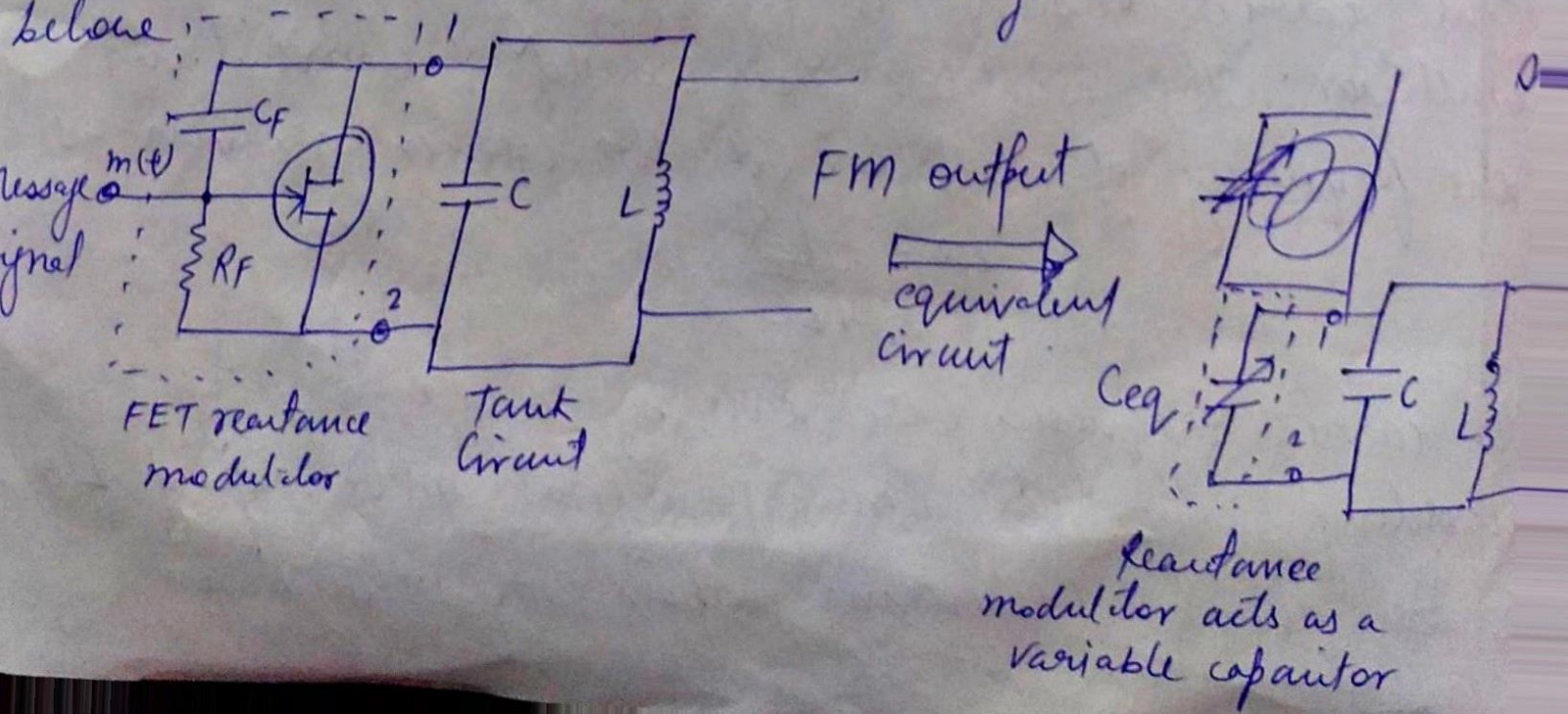The basic reactance modulator using FET is shown below:




Assumption made are -

① $i_b \ll i_d$, ② $X_c \gg R$

From the figure

$$V_g = i_b \cdot R$$
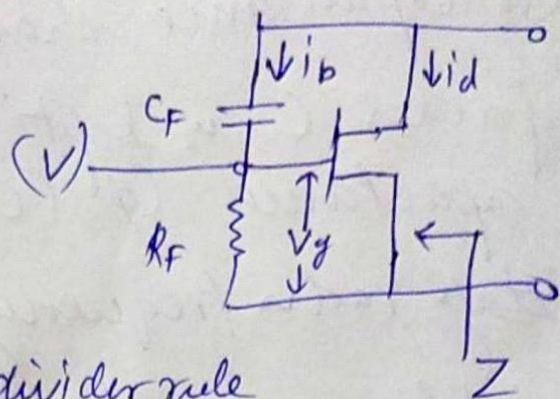
$$= V \cdot \frac{R_F}{R_F - jX_{CF}} \quad \text{using voltage divider rule}$$



Transconductance of FET $g_m = \frac{i_d}{V_g}$

$$\Rightarrow i_d = g_m \cdot V_g = g_m \cdot \frac{V \cdot R_F}{R_F - jX_{CF}}$$

Since $i_b \ll i_d$, then $Z = \frac{V}{i_d}$

$$\Rightarrow Z = \frac{V}{g_m \cdot \frac{V \cdot R_F}{R_F - jX_{CF}}} = \frac{R_F - jX_{CF}}{g_m \cdot R_F} = \frac{1}{g_m} \left[1 - \frac{jX_c}{R_F} \right]$$

$$Z = -\frac{1}{g_m} \left[j \frac{X_c}{R_F} - 1 \right]$$

Since $X_c \gg R_F$ hence impedance $Z = \frac{-jX_{CF}}{g_m \cdot R_F}$

& $X_{CF} = \frac{1}{2\pi f C_F}$

$$\Rightarrow Z = j \frac{1}{2\pi f \cdot C_F \cdot g_m \cdot R_F} = -j X_{eq} \quad \text{--- ①}$$


where $X_{eq} = \frac{1}{2\pi f \cdot C_{eq}}$ and $C_{eq} = C_F \cdot g_m \cdot R_F$

From eq - ①, it can be Z (impedance) is capacitive in nature and its capacitance $C_{eq} = g_m \cdot R_F \cdot C_F$

b) - Varactor diode method for FM generation

The varactor diode is a semi-conductor device whose junction capacitance changes with d.c. bias voltage. The capacitor C is kept much smaller than the diode capacitance C_d ($C \ll C_d$). In order to keep the ~~voltage~~ radio frequency (R.F.) voltage from the oscillator across the diode small as compared to the reverse bias d.c. voltage.

Working Principle

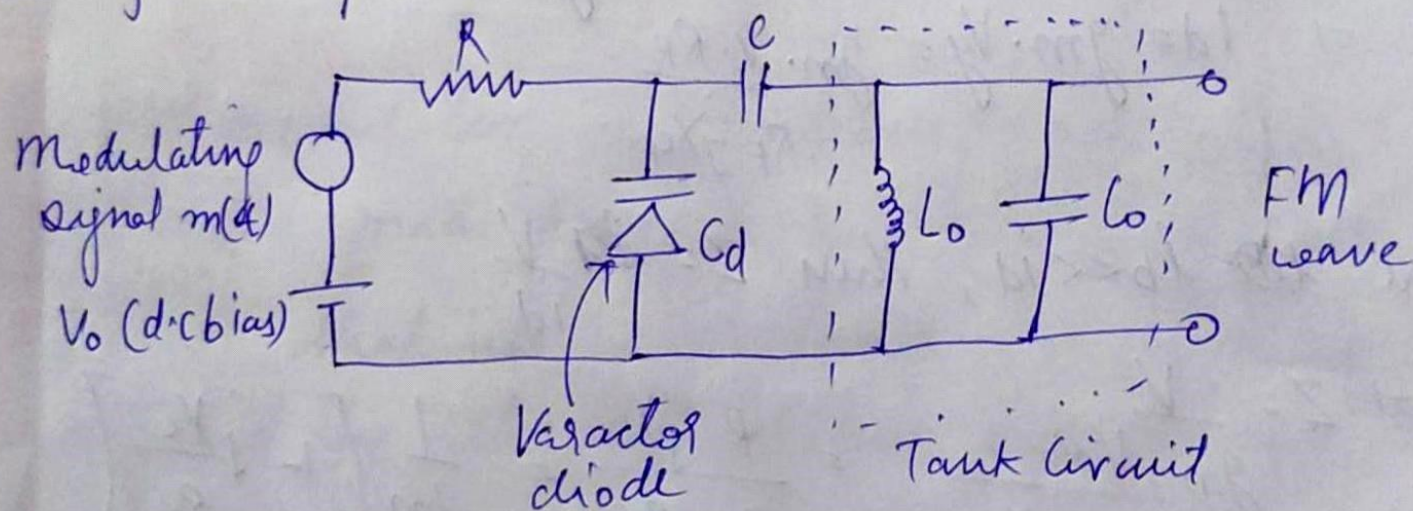

Total voltage applied to the varactor diode is $V_d = V_0 + m(t)$

V_d = instantaneous voltage across varactor diode
 Relation b/w junction capacitance and applied voltage across varactor diode is $C_d \propto \frac{1}{\sqrt{V_d}}$
 or $C_d = k \cdot V_d^{-1/2}$

$$= k [V_0 + m(t)]^{-1/2}$$

where k is proportionality constant

Total capacitance = $C_0 + C_d + C$
 since $C \ll C_d$
 $= C_0 + C_d$

hence instantaneous frequency of oscillation

~~$\omega_i = \frac{1}{\sqrt{L_0 C_0}}$~~ $\omega_i = \frac{1}{\sqrt{L_0 (C_0 + C_d)}}$

$\Rightarrow \omega_i = \frac{1}{\sqrt{L_0 (C_0 + k[V_0 + m(t)]^{1/2})}}$

here ω_i is dependant upon the message signal $m(t)$
 and hence frequency modulated wave is generated

Disadvantages of Direct method

① In this method, it is difficult to obtain the stability at high carrier frequency.

② In varactor diode method ω_i varies non-linearly with $m(t)$ which causes instability.