

# AC Bridge

For DC :- Capacitor act as - open circuit  
or we can say that  
the resistance is  $\infty$   
we can also say that capacitor  
blocks DC

:- Inductor act as - Short circuit  
or its resistance is 0  
we can say that inductor  
passes DC without any  
attenuation

For AC :-  $R \rightarrow R$

Capacitor  $\rightarrow$  Capacitance  
 $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

$$X_C \propto \frac{1}{f}$$

Inductor  $\rightarrow$  Inductance

$$X_L = \omega L = 2\pi f L$$

$$X_L \propto f$$

Impedance को हम 2 notation से define कर सकते हैं

$\xrightarrow{\quad}$   
 $\searrow$

Rectangular form

Polar form

→ Rectangular form:-


$2 + 2j$  or  $2 - 2j$  & magnitude and phase both are present

→ Notation with j

$R \rightarrow R$


Capacitance  $\rightarrow X_C \rightarrow -jX_C$

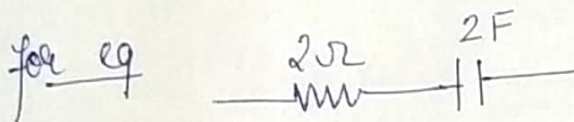Inductance  $\rightarrow X_L \rightarrow +jX_L$



$2 - 2j$

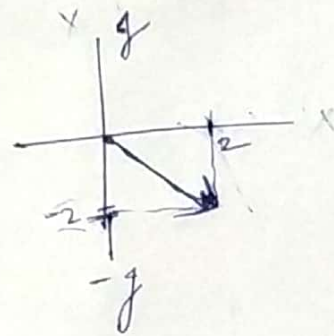Magnitude  $\rightarrow \sqrt{2^2 + 2^2}$   
 $= \sqrt{8} \Rightarrow 2\sqrt{2}$



phase  $\rightarrow \tan \theta = \frac{-2}{2} = -1$

$\theta = \tan^{-1}(-1)$

$= -\tan^{-1}(1) = -\tan^{-1}(\tan 45) = -45$

$\theta = -ve$  capacitive

$\theta = +ve$  inductive

→ Polar form:-


$Z \angle \theta$

$2\sqrt{2} \angle -45$

$2 + 2j$  को directly magnitude & phase में लिखा है जो है polar form में लिखा है।



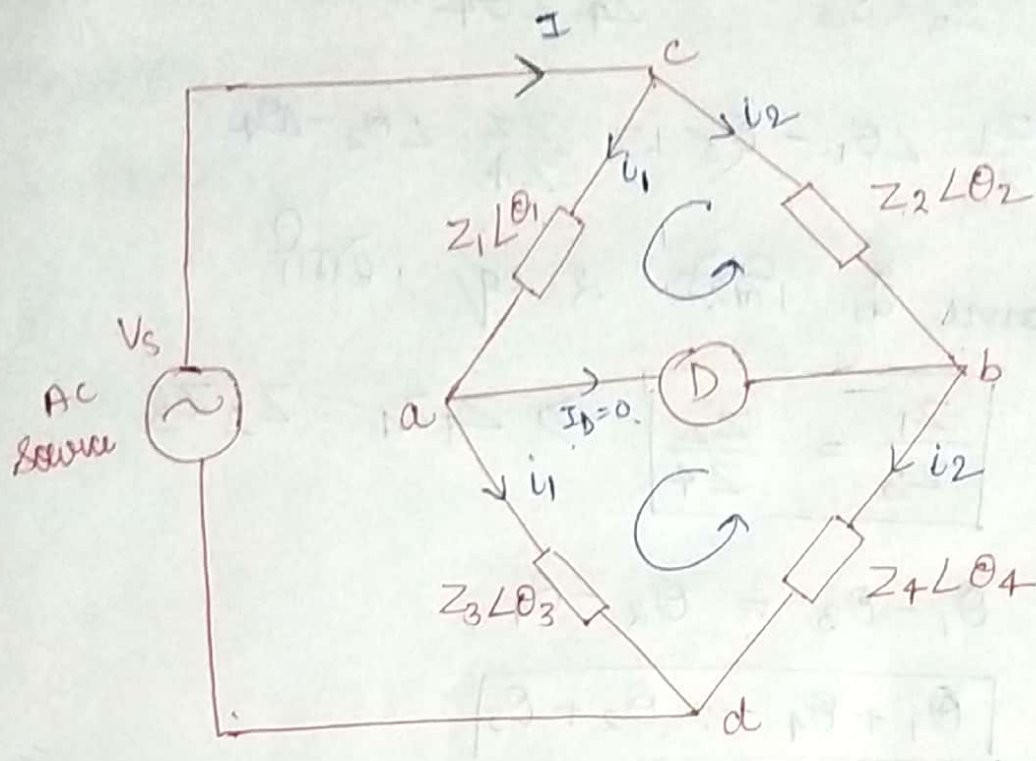Inductance, Capacitance,  $\phi$ -factor, frequency  
 ये सभी AC bridges द्वारा measure  
 किया जा सकता है।



$Z \angle \theta$

$\hookrightarrow$  impedance का magnitude  
 $\hookrightarrow$  impedance का phase

In null condition i.e. when current in the detector is 0 ( $I_D = 0$ ) the point a & b are at same voltage

Applying KVL in c a b c

$$i_1 (Z_1 \angle \theta_1) + 0 - i_2 (Z_2 \angle \theta_2) = 0$$

$$i_1 (Z_1 \angle \theta_1) = i_2 (Z_2 \angle \theta_2) \quad \text{--- (1)}$$

Applying KVL in a d b a

$$i_1 (Z_3 \angle \theta_3) - i_2 (Z_4 \angle \theta_4) + 0 = 0$$

$$i_1 (Z_3 \angle \theta_3) = i_2 (Z_4 \angle \theta_4) \quad \text{--- (2)}$$

from eq ① & ② को divide करने पर

$$\frac{Z_1 \angle \theta_1}{Z_3 \angle \theta_3} = \frac{Z_2 \angle \theta_2}{Z_4 \angle \theta_4}$$

$$\frac{Z_1}{Z_3} \angle \theta_1 - \theta_3 = \frac{Z_2}{Z_4} \angle \theta_2 - \theta_4$$

so, Balance के लिये 2 eq होगा

$$\boxed{\frac{Z_1}{Z_3} = \frac{Z_2}{Z_4}} \Rightarrow Z_1 Z_4 = Z_2 Z_3$$

$$\theta_1 - \theta_3 = \theta_2 - \theta_4$$

$$\therefore \boxed{\theta_1 + \theta_4 = \theta_2 + \theta_3}$$

For Rectangular co-ordinate

$$Z_1 = R_1 + jX_1$$

$$Z_3 = R_3 + jX_3$$

$$Z_2 = R_2 + jX_2$$

$$Z_4 = R_4 + jX_4$$

for balanced condition

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + jX_1)(R_4 + jX_4) = (R_2 + jX_2)(R_3 + jX_3)$$

$$\begin{aligned} (R_1 R_4 - X_1 X_4) + j(R_1 X_4 + X_1 R_4) = \\ (R_2 R_3 - X_2 X_3) + j(X_2 R_3 + R_2 X_3) \end{aligned}$$



यह eq एक complex eq है और यह तभी satisfy होगी जब इसके दोनों sides के real or imaginary parts अलग-अलग equal हो गे।

∴ Balance के लिये -

$$R_1 R_4 - X_1 X_4 = R_2 R_3 - X_2 X_3 \quad \text{--- real part}$$

$$R_1 X_4 + X_1 R_4 = X_2 R_3 + R_2 X_3 \quad \text{--- imaginary}$$