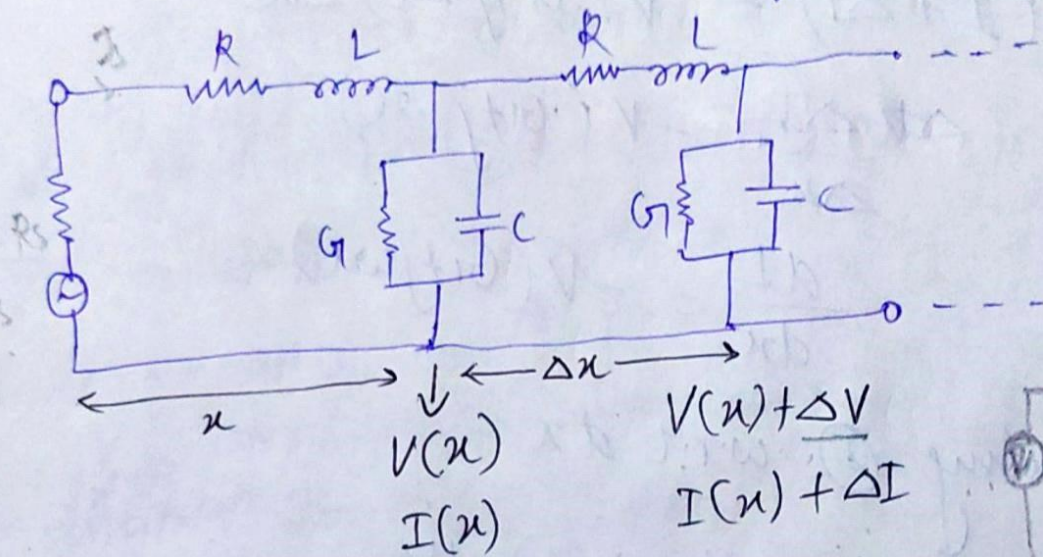


Transmission Lines Equations

- Let the length of the transmission line be ' l ', and the primary constants be R , L , G , and C .
- A small section of the line 'XY' is considered, of length Δx , and at a distance of ' x ' from source.



Considering a small section Δx

$$\text{series impedance} = (R + j\omega L) \Delta x$$

$$\text{shunt admittance} = (G + j\omega C) \Delta x$$

→ Voltage drop occurs due to elements in series of the voltage ~~so~~ circuit.

→ Current drop occurs due to elements in shunt arm of the circuit.

So drop in voltage, will be

$$V - (V + \Delta V) = I(R + j\omega L) \Delta x$$

$$-\Delta V = I(R + j\omega L) \Delta x$$

$$= \frac{\Delta V}{\Delta x} = \frac{dV}{dx} = -(R + j\omega L)I \quad \text{--- (1)}$$

and similarly drop in current

$$I - (I + \Delta I) = V(G + j\omega C) \Delta x$$

$$\frac{\Delta I}{\Delta x} = -V(G + j\omega C)$$

$$\frac{dI}{dx} = -V(G + j\omega C) \quad \text{--- (2)}$$

Differentiating (2) w.r.t dx

$$\frac{d^2 I}{dx^2} = -(G + j\omega C) \frac{dV}{dx}$$

putting (1) in above equation

$$\frac{d^2 I}{dx^2} = (G + j\omega C)(R + j\omega L)I$$

let $\gamma^2 = (G + j\omega C)(R + j\omega L)$, then

$$\boxed{\frac{d^2 I}{dx^2} = \gamma^2 I}$$

differentiating ① and putting ① into it, will result into

$$\boxed{\frac{d^2 V}{du^2} = \gamma^2 V}$$

On simplifying $\frac{d^2 V}{du^2} - \gamma^2 V = 0$ is a general form of differential equation and its solution can be obtained as

$$V = A \cdot e^{\gamma x} + B \cdot e^{-\gamma x}$$

$$e^{\gamma x} = e^{\gamma u} = \cosh(\gamma u) + \sinh(\gamma u)$$

$$e^{-\gamma x} = \cosh(\gamma u) - \sinh(\gamma u)$$

$$V = A(\cosh(\gamma u) + \sinh(\gamma u)) + B(\cosh(\gamma u) - \sinh(\gamma u))$$

$$V = (A+B)\cosh(\gamma u) + (A-B)\sinh(\gamma u)$$

$$V = a \cosh(\gamma u) + b \sinh(\gamma u)$$

—(3)

where $a = A+B$, $b = A-B$

$$\frac{dV}{du} = a \cdot \gamma \sinh(\gamma u) + b \cdot \gamma \cosh(\gamma u)$$

Following similar $I = \frac{-1}{(R+j\omega L)} \frac{dV}{du}$

$$I = \frac{-1}{(R+j\omega L)} \cdot [a \cdot \gamma \cdot \sinh(\gamma u) + b \cdot \gamma \cosh(\gamma u)]$$

or $\gamma^2 = (R+j\omega L)(G+j\omega C)$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$I = - \sqrt{\frac{G+j\omega C}{R+j\omega L}} [a \sinh(\gamma u) + b \cosh(\gamma u)]$$

$$Z_0 = \sqrt{\frac{Rj\omega L}{Gj\omega C}}$$

$$I = -\frac{1}{Z_0} [a \sinh(rn) + b \cosh(rn)] \quad \text{--- (4)}$$

at $n=0$, $I = I_s$, $V = V_s$. $I_s = -\frac{b}{Z_0}$

from (6), at $n=0$, $V = V_s$.

$$\Rightarrow a = V_s$$

from (4) at $n=0$, $I = I_s$.

$$I_s = -\frac{b}{Z_0} \quad b = -I_s Z_0$$

then $V = V_s \cdot \cosh(rn) - I_s Z_0 \sinh(rn)$

$$I = I_s \cdot \cosh(rn) - \frac{V_s}{Z_0} \sinh(rn)$$

at a distance of 'n' from the source
then

at $n=l$.

$$V = V_L \cdot \cosh(rL) - I_L \cdot Z_0 \sinh(rL)$$

$$I = I_L \cosh(rL) - \frac{V_L}{Z_0} \sinh(rL)$$