

Attenuation & Phase constant

$$\gamma = \alpha + j\beta$$

$\alpha \rightarrow$ attenuation constt.
 $\beta \rightarrow$ phase constt.

$$\alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Squaring

$$\alpha^2 - \beta^2 + 2j\alpha\beta = (R + j\omega L)(G + j\omega C)$$

$$\alpha^2 - \beta^2 + 2j\alpha\beta = RG - \omega^2 LC + j\omega(LG + RC)$$

Comparing real & imaginary parts

$$\alpha^2 - \beta^2 = RG - \omega^2 LC \quad \text{--- (1)}$$

$$2\alpha\beta = \omega(LG + RC) \quad \text{--- (2)}$$

mag magnitude of γ , $|\gamma| = \sqrt{\alpha^2 + \beta^2}$

$$|\gamma| = \sqrt{\sqrt{R^2 + (\omega L)^2} \sqrt{G^2 + (\omega C)^2}}$$

$$= \sqrt{\alpha^2 + \beta^2} = \sqrt{\sqrt{R^2 + \omega^2 L^2} \sqrt{G^2 + \omega^2 C^2}}$$

$$\Rightarrow \alpha^2 + \beta^2 = \sqrt{R^2 + \omega^2 L^2} \sqrt{G^2 + \omega^2 C^2} \quad \text{--- (3)}$$

Adding (1) and (3)

$$2\alpha^2 = \sqrt{R^2 + \omega^2 L^2} \sqrt{G^2 + \omega^2 C^2} + RG - \omega^2 LC$$

$$\alpha = \sqrt{\frac{1}{2} \left\{ \sqrt{R^2 + \omega^2 L^2} \sqrt{G^2 + \omega^2 C^2} + RG - \omega^2 LC \right\}}$$

Subtracting (3) from (1)

$$2\beta^2 = \frac{\sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} - (RG - \omega^2 LC)}{1}$$

$$\beta = \sqrt{\frac{1}{2} \left\{ \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} - (RG - \omega^2 LC) \right\}}$$

distortions in Transmission line

→ When the transmitted wave and the received wave at the load are NOT the exact same replica (copy) of each other, then we say the transmission line is having distortions.

→ The major causes of ~~at~~ the distortion in a transmission line is the presence of multiple frequency components.

Major causes of distortions in transmission line.

① - Characteristic impedance (Z_0) varying with frequency.

→ The characteristic impedance is a function of frequency and it changes with frequency.

→ When the transmission line is terminated with a ~~load~~ impedance, which does not change with the frequency and multiple frequency components, like the characteristic impedance, then it leads to distortion.

② Frequency distortion.

The attenuation constant, α , is the measure of attenuation in an electromagnetic wave travelling from source to the load.

→ α is a function of frequency. Thus multiple frequency terms will have attenuation to different levels.

→ Such a distortion is called frequency distortion.


③ Delay distortion.

→ The propagation velocity of a wave is given as

$$v = \omega / \beta, \quad \beta \rightarrow \text{phase constant.}$$

→ β is a function of frequency and changes rapidly with ~~freq~~ change in frequency.

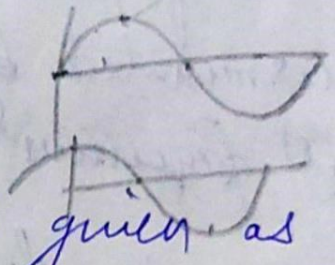→ Due to this, the velocity of the wave also changes with the frequency. and the transmitting time for all waves will NOT be the same.



Condition for minimum distortion

① Reducing change in Z_0 with the change in frequency.

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$= \sqrt{\frac{R(1 + j\omega \frac{L}{R})}{G(1 + j\omega \frac{C}{G})}}$$

$$\frac{L}{R} = \frac{C}{G}$$

if $\frac{L}{R} = \frac{C}{G}$, then

$$Z_0 = \sqrt{\frac{R}{G}}$$

→ For $\frac{L}{R} = \frac{C}{G}$, the characteristic impedance is

independent of frequency, and is completely resistive in nature.

→ Thus for this case, the transmission line can be terminated by Z_0 , and will reduce distortion at all frequencies.

② Reducing change in attenuation constant with frequency

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma = \sqrt{RG(1 + j\omega \frac{L}{R})(1 + j\omega \frac{C}{G})}$$

if $\frac{L}{R} = \frac{C}{G}$, then

$$\gamma = \sqrt{RG \left(1 + j\omega \frac{L}{R}\right)^2}$$

$$\gamma = \sqrt{RG} \left(1 + j\omega \frac{L}{R}\right)$$

$$\gamma = \sqrt{RG} + j\omega L \sqrt{\frac{G}{R}}$$

$$\gamma = \sqrt{RG} + j\omega L \sqrt{\frac{C}{L}}$$

$$\gamma = \sqrt{RG} + j\omega \sqrt{LC}$$

$$\left[\frac{RL}{R} = \frac{GL}{G} \right] \\ \Rightarrow \frac{G}{R} = \frac{C}{L}$$

also $\gamma = \alpha + j\beta$

on comparing $\alpha = \sqrt{RG}$, $\beta = \omega \sqrt{LC}$

→ Here α , is independent of frequency, and so, change in attenuation of different wave having different frequencies will NOT occur.

③ Reducing distortion due to velocity varying with frequency.

$$v = \frac{\omega}{\beta}$$

→ Above we have derived that

$$\beta = \omega \sqrt{LC} \text{ for the condition } \frac{L}{R} = \frac{C}{G}$$

So velocity of wave, in this case

$$v = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

→ Since ω , is independent of frequency, so all the waves will travel with same speed and there will be no delay.