

## Multi stage Amplifier

- The o/p from a single stage amp<sup>r</sup> is usually insufficient to drive a o/p device.
- In other words, the gain of single stage amp<sup>r</sup> is not enough for practical purpose. So, more than one amp stage amplification is required.
- To achieve the o/p of one stage is coupled with i/p of next stage. The resulting system is referred as Multistage amp<sup>r</sup>.
- For ex - In a transistor radio receiver, the no of amplification stage is six or more.


## Multi stage Transistor Amp<sup>r</sup>

A transistor circuit containing more than one stage of amplification is known as Multistage Transistor amp<sup>r</sup>.

In a multi stage amp<sup>r</sup>, a no of single stage amp<sup>r</sup> are connected in cascade arrangement. (O/p of one stage is connected to i/p of next stage).



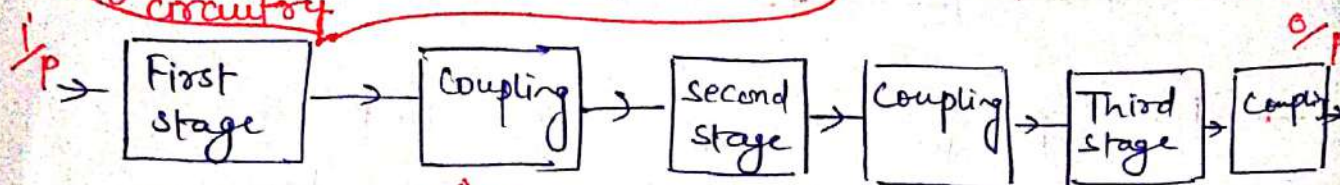Each stage consist of one transistor & associated circuitry.



The purpose of coupling device

- i) Transfer A.C  $\& p$  to next stage
- ii) To isolate DC from next stage.

Name of coupling

Rc coupling

Transformer coupling

Direct coupling

Name of multistage Amp<sup>r</sup>

Rc coupled Amp<sup>r</sup>

Transformer coupled Amp<sup>r</sup>


Direct coupled Amp<sup>r</sup>.

Rc coupled Transistor Amp<sup>r</sup>

In Rc coupled amp<sup>r</sup>, Capacitor is used as coupling device.

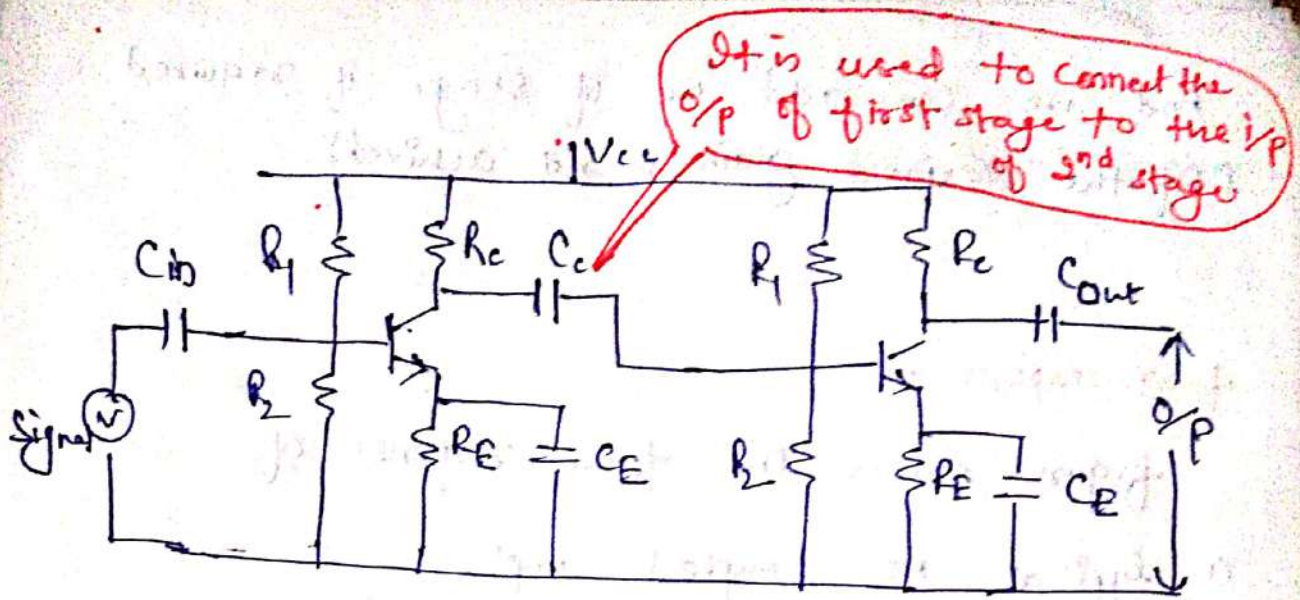- This is the most popular type of coupling because it is cheap & provides excellent audio fidelity over a wide range of freq.
- usually used for voltage amplification.





- $R_1$ ,  $R_2$  &  $R_E$  form the biasing & stabilization network.
- $C_E$  offers low reactance path to the signal.
- $C_c$  transmits A.C signal but blocks D.C which prevents DC interface between stages.

As the coupling from one stage to next stage is achieved by coupling capacitor followed by shunt resistors, therefore such amp<sup>r</sup> is called resistance-capacitance coupled amp<sup>r</sup>.

### Operation -


- When AC signal is applied to the base of first transistor, it appears in amplified form across its collector load  $R_C$ .
- The amplified signal developed across  $R_C$  is given to base of next stage through  $C_c$ .
- The second stage does further amplification of the signal.
- In this way, the cascade connection (one after another) & with no of stages amplifies the signal.



And we can add no. of stage if required (if the desired gain is not achieved).

**freq. response —**

figure shows the freq. response of a typical RC coupled amp<sup>r</sup>.

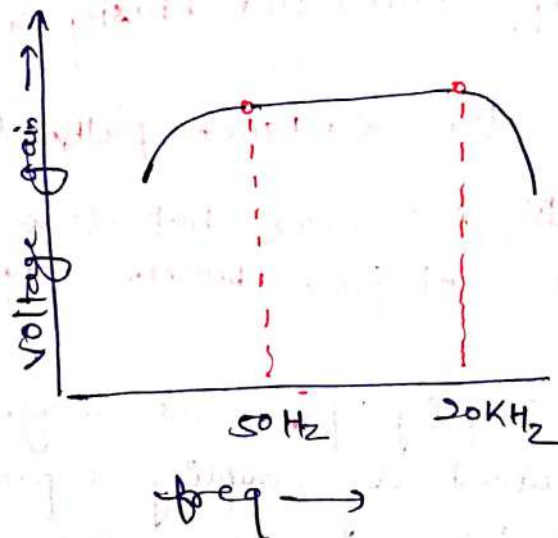

**At Low freq.** At ( $< 50 \text{ Hz}$ ), the reactance of  $C_e$  is quite high, and hence very small part of signal will pass from one stage to next.

**At High freq.** — At high freq ( $> 20 \text{ KHz}$ ) the reactance of  $C_e$  is very small & it behaves as a s.c. This increases the loading effect of next stage & serve to reduce the voltage gain.

**At mid freq. ( $50 \text{ Hz}$  to  $20 \text{ KHz}$ ).** — Here the voltage gain of amp<sup>r</sup> is constant.



### Advantages -

Very cost effective (as resistors & capacitors are very cheap).

### Disadvantage -

Impedance Matching is poor & has low voltage gain.

### Transformer Coupled Amp<sup>r</sup>

In Transformer coupled amp<sup>r</sup> Transformer is used for coupling.


The Benefit with Transformer is high voltage gain & high power gain.

→ This is due to in RC coupled amp<sup>r</sup> the effective load ( $R_{AC}$ ) of each stage is decreased due to low resistance presented by  $i_p$  of each stage to preceding stage.

→ In other words,  $i_p$  impedance of  $i_p$  amp<sup>r</sup> is low while its  $o_p$  impedance is high.

→ & when they are coupled to make multistage amp<sup>r</sup>, the high  $o_p$  impedance of one stage comes in || with low  $i_p$  impedance of next stage. Hence effective load is decreased. This prob can be overcome by Transformer coupled amp<sup>r</sup>.



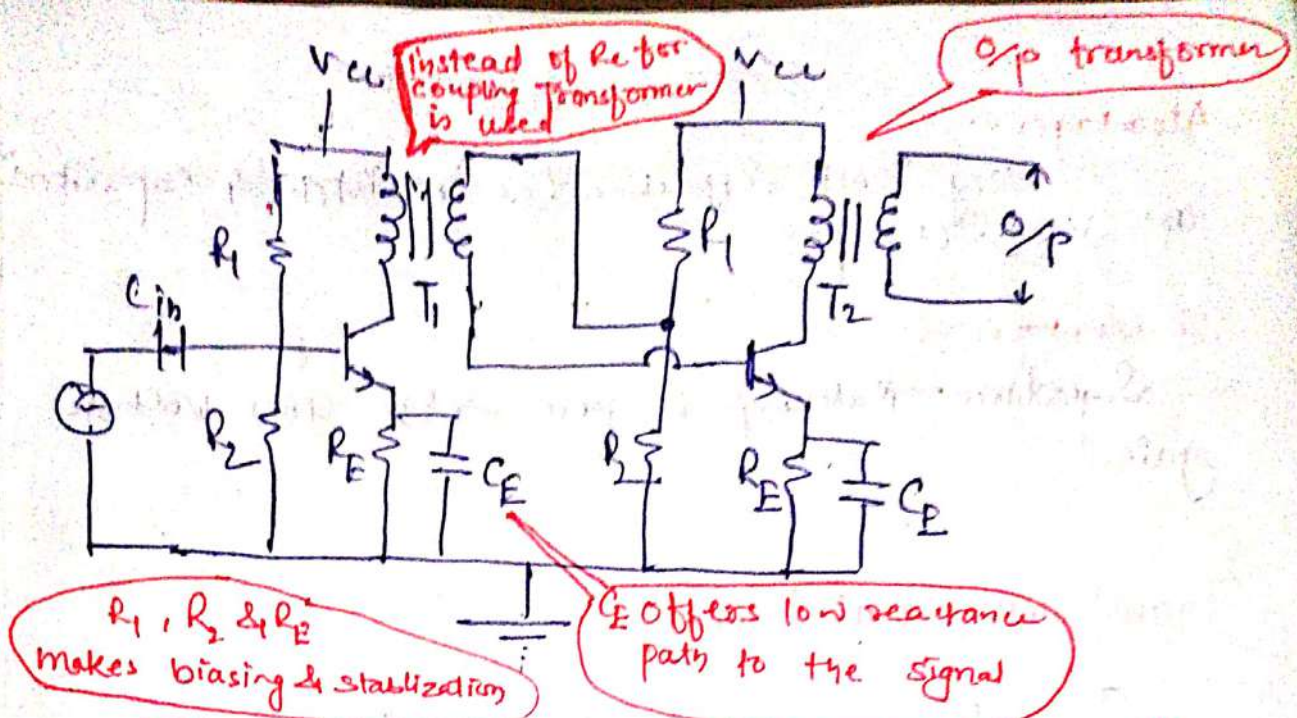

- $T_1$  is used to feed the o/p of 1<sup>st</sup> stage to i/p of 2<sup>nd</sup> stage.
- $R_E$  is replaced by primary winding of  $T_1$  & secondary winding is connected between potential divider ( $R_1$  &  $R_2$  of 2<sup>nd</sup> stage) & base of 2<sup>nd</sup> stage.
- When AC signal is applied to the i/p of the base of 1<sup>st</sup> transistor then it gets amplified by transistor & appears at the collector which is primary winding of Transformer.
- Transformer which is used as a coupling device in the circuit has a property of impedance changing (because of turn ratio).
- Means resistance of a stage can be reflected as high load resistance to the previous stage.
- So, Transformer coupling provides good impedance b/w the stages of amp.



## freq response of Transformer Coupled Amp


At low freq, the reactance of primary begins to fall, resulting in decreased gain.

At high freq, the capacitance b/w turns of winding acts as bypass condenser to reduce the o/p voltage & hence gain.

So, the amplification of audio signals will not be proportionate & some distortion will also get induced, which is called freq. distortion.
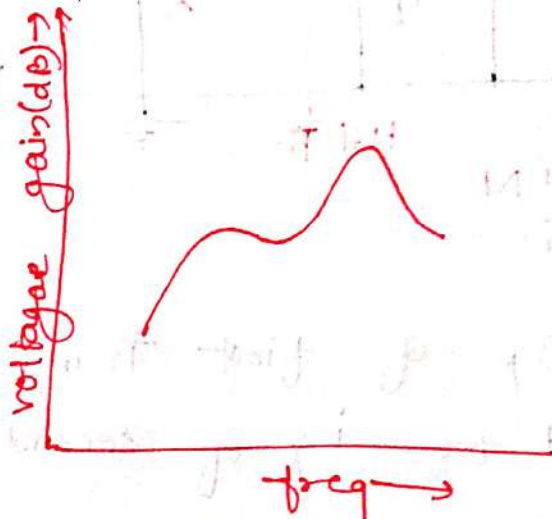
### Advantage

- Gain Achieved is higher
- An excellent impedance matching is provided.



### Disadvantage

- Bulky & costly due to use of Transformer.
- Freq. distortion is higher


### Application

- Mostly used for impedance matching.
- used for Power amplification.



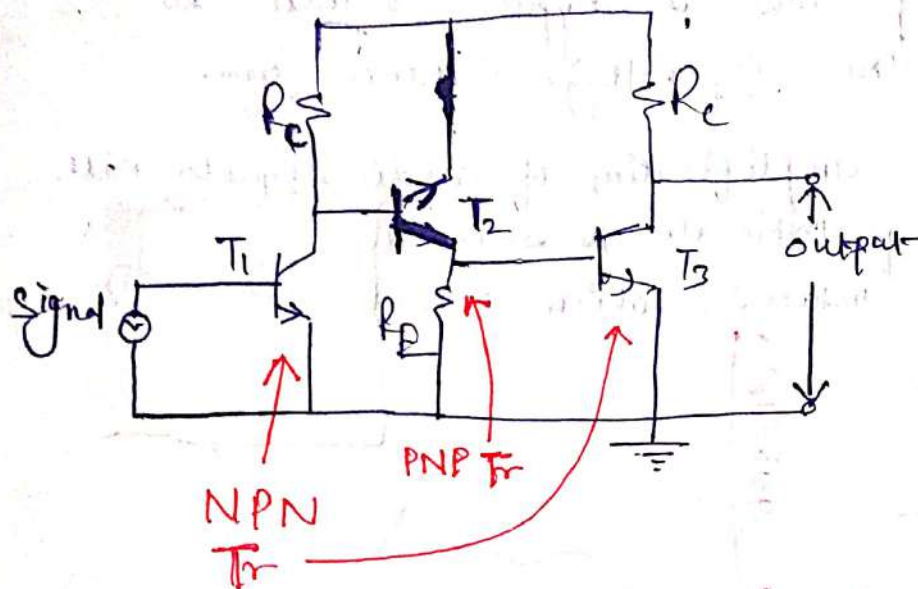
## Directly Coupled Amp

The other type coupling amp is direct coupled amp. It is especially used to amplify lower freq.



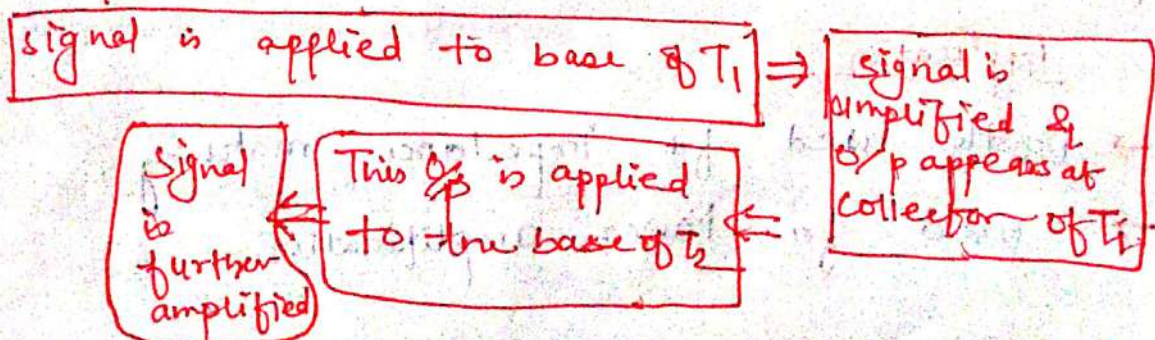- The o/p of first transistor  $T_1$  is connected to i/p of second stage  $T_2$
- The Variation of one transistor tend to cancel the variation in other
- The rise in the collector current &  $\beta$  of one transistor is cancelled by other transistor
- operation





### Advantage

- The circuit is simple because of minimum use of resistor.
- Cost effective because of min no of components use & no use of Transformer.

### Disadvantage

- It can't be used for high freq.
- The operating point is shift due to temp.

### Application

- Low freq application
- Low current application.

### Comparison

S. No.	Particular	RC coupling	Transformer coupling	Direct coupling
01.	Freq. Response	Excellent in audio freq. range	Poor	Best
02.	Cost	Less	More	Least
03.	Space & weight	Less	More	Least
04.	Impedance matching	not good	Excellent	good
05.	Use	used for voltage amplification	For Power amplification	for very low freq.



Goklani

R. Goklani